

Electricity- Potential Dividers Past Paper Answers AQA Physics A Level

1.

1	energy of <u>photon</u> ✓ is greater than the work function ✓ so electrons are emitted ✓	If correct reference to threshold frequency and no mention of work function then only score one of first two marks and can be awarded third mark	1 1 1
2	increased intensity means more photons incident per second ✓ current greater OR more electrons emitted per second ✓	only need to see per second once rate of photons incident OK (or rate of electrons emitted)	1 1
3	(use of $hf = \phi + E_k$) $\phi = 2.1 \times 1.6 \times 10^{-19} = 3.36 \times 10^{-19}$ ✓(J) $E_k = 6.63 \times 10^{-34} \times 7.23 \times 10^{14} - 3.36 \times 10^{-19}$ ✓ $E_k = 1.4(3) \times 10^{-19}$ ✓(J)	If incorrect or no conversion to J then CE for next two marks	1 1 1
4	(use of $eV = E_k$) $V_s = 1.43 \times 10^{-19} / 1.6 \times 10^{-19} = 0.89$ (V) ✓	CE from 05.3 RANGE 0.70 – 0.90	1
5	stopping potential would be greater ✓ because the <u>energy</u> of the <u>photons</u> (of the electromagnetic radiation) would be greater ✓ (hence) <u>maximum</u> kinetic energy of (photo)electrons would be greater ✓		1 1 1

2.

(a)	(use of $1/R_{\text{total}} = 1/R_1 + 1/R_2$) $1/R_{\text{total}} = 1/400 + 1/400 = 2/400$ $R_{\text{total}} = 200 \Omega$ ✓ (working does not need to be shown) hence total resistance = $25 + 200 = 225 \Omega$ ✓	2
(b) (i)	(use of $P = V^2/R$) $1 = V^2/400$ ✓ $V^2 = 400$ (working does not need to be shown) $V = 20 \text{ V}$ ✓	6
(ii)	(use of $I = V/R$) $I = 20/400 = 0.05 \text{ A}$ ✓ (working does not need to be shown) hence current = $2 \times 0.05 = 0.10 \text{ A}$ ✓	
(iii)	(use of $V = IR$) pd across 25Ω resistor = $25 \times 0.10 = 2.5 \text{ V}$ ✓ (working does not need to be shown) hence maximum applied pd = $20 + 2.5 = 22.5 \text{ V}$ ✓	
	Total	8

3.

(a)	(i)	$6.0 (\Omega) \checkmark$	1
(a)	(ii)	$4.5 (V) \checkmark$	1
(a)	(iii)	(use of $I = V/R$) $I = 4.5/6.0 = 0.75 (A) \checkmark$ current through cell A = $0.75/2 = 0.375 (A) \checkmark$	2
(a)	(iv)	charge = $0.375 \times 300 = 112 \checkmark C \checkmark$	2
(b)		cells C and D will go flat first or A and B last longer \checkmark current/charge passing through cells C and D (per second) is double/more than that passing through A or B \checkmark energy given to charge passing through cells per second is double or more than in cells C and D \checkmark or in terms of power	3
Total			9

4.

(a)		current = $0.40 A \checkmark$	1
(b)	(i)	resistance = $12/0.2 = 60 \Omega \checkmark$	1
(b)	(ii)	power = $12 \times 0.2 = 2.4 W \checkmark$	1
(c)		resistance of filament increases or more collisions/scattering \checkmark as temperature of filament increase or filament gets hot/heats (until reaches thermal equilibrium) \checkmark	2
(d)	(i)	voltage of supply now shared by lamps or resistance increased \checkmark hence current reduced \checkmark	2
(d)	(ii)	current through the lamps unchanged/stays the same \checkmark as both connected directly to the supply or correct resistance argument \checkmark	2
(e)		resistance of lamps will be lower when first switched on \checkmark hence initial current will be larger \checkmark sudden rapid change in temperature \checkmark	max 2
Total			11

5.

a	(i)	$1/R_{\text{total}} = 1/(40) \checkmark + 1/(10+5) \checkmark = 0.09167$ $R_{\text{total}} = 10.9 \text{ k}\Omega \checkmark$		3	
a	(ii)	$I = 12/10.9\text{k} = 1.1 \text{ mA} \checkmark$		1	
b		position	pd/V	3	C.E. for CD
		AC	6.0 \checkmark		
		DF	4.0 \checkmark		
		CD	2.0 \checkmark		
c	(i)	AC: no change \checkmark constant pd across resistors/parallel branches(AE) \checkmark		2	no CE from first mark
c	(ii)	DF: decreases \checkmark as greater proportion of voltage across fixed/10 k Ω resistor \checkmark		2	no CE from first mark