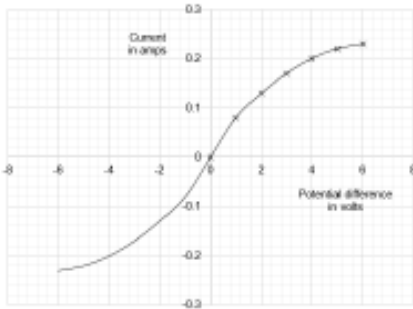
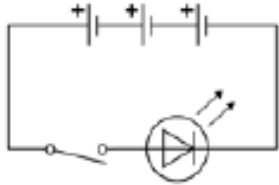


ElectricityPast Paper Answers AQA Physics GCSE

| Question | Answers  | Extra information  | Mark                         |
|----------|--|--|------------------------------|
| 1        | ammeter and voltmeter symbols correct<br><br>voltmeter in parallel with lamp<br><br>ammeter in series with lamp  |  | 1<br><br>1<br><br>1          |
| 2        | smooth curved line of correct shape<br><br>passing through - 4.0 V, - 0.2 A<br>or<br>- 6.0 V, - 0.23 A<br><br> | do not accept a line that becomes horizontal<br><br>2 <sup>nd</sup> mark conditional on scoring 1 <sup>st</sup> mark   | 1<br><br>1                   |
| 3        | potential difference = current × resistance<br>or<br>$V = IR$  |  | 1                            |
| 4        | $I = 0.08 \text{ (A)}$<br>$1.0 = 0.08 \times R$<br><br>$R = \frac{1.0}{0.08}$<br><br>$R = 12.5 \text{ (}\Omega\text{)}$  | allow $1.0 = \text{their } I \times R$ provided their $I$ has been obtained from the graph<br><br>allow $R = \frac{1.0}{\text{their } I}$<br><br>allow an answer consistent with their $I$ | 1<br><br>1<br><br>1<br><br>1 |

| Question | Answers  | Extra information | Mark |
|----------|--|-------------------|------|
| 5        | ammeter displays a reading when not connected (to a circuit) |                   | 1    |

| Question | Answers   | Extra information   | Mark        |
|----------|---|---|-------------|
| 6        |    |   | 1           |
| 7        | charge flow = current $\times$ time<br>or<br>$Q = It$   |   | 1           |
| 8        | $I = 0.050$ (A)<br>$Q = 0.050 \times 14\ 400$<br>$Q = 720$ (C)  | allow a correct substitution using an incorrectly/not converted value of I<br><br>allow a correct calculation using an incorrectly/not converted value of I | 1<br>1<br>1 |
| 9        | there is no current in a diode (in the reverse direction)<br>or<br>charge will not flow through a diode (in the reverse direction)<br><br>(because) a diode has a (very) high resistance (in the reverse direction) | allow diode will not conduct (electric charge)<br><br>do not accept the circuit is not complete   | 1<br><br>1  |
| 10       | $\text{Efficiency} = \frac{\text{Useful power output}}{\text{Total power input}}$   |   | 1           |

| Question | Answers  | Extra information | Mark |
|----------|--|-------------------|------|
| 11       | $0.75 = \frac{\text{Useful power output}}{0.24}$ |                   | 1    |
|          | Useful power output = $0.75 \times 0.24$         |                   | 1    |
|          | Useful power output = 0.18 (W)                   |                   | 1    |