

Electricity Past Paper Answers Edexcel Physics IGCSE -Higher


1.

Question number	Answer	Notes	Marks
1 (a) (i)	A		1
(ii)	B		1
(b) (i)	C		1
(ii)	nearest above (DOP)		1
(iii)	Comment on device – (plastic) insulator / does not conduct;	(double) insulated / no current (through) / cannot become live	1
	Comment on user - no risk of shock / electrocution;	No electricity reaches user / person cannot touch live parts	1

2.

Question number	Answer	Notes	Marks
(a)	CIRCUIT DIAGRAM – Correct symbols for ammeter, voltmeter and battery; Ammeter in series with cells;	ALLOW three separate cells in series	1
	Voltmeter in parallel with wire / as shown in photograph;	ALLOW anything reasonable for the wire (e.g. straight line, variable resistor, resistor)	1
(b) (i)	(independent variable) – length (of wire) (dependent variable) - resistance	BOTH NEEDED	1
(ii)	ANY FIVE APPROPRIATE, e.g. Connect the circuit / connect (crocodile) clip to wire; Read ammeter; Read voltmeter; For known /particular / quoted value length; measure length with a ruler; Repeat readings / average (in different places along the wire); Take readings for different lengths; Check meters for zero errors; Disconnect/switch off between readings; To avoid heating the wire;	IGNORE references to calculating resistance, plotting graphs –	5

Question Number	Answer	Notes	Marks
(c) (i)	Voltage = current x resistance;	ALLOW standard symbols, $V = I \times R$ ALLOW correct rearrangements DO NOT ALLOW equation given as unit symbols	1
(ii)	6.4;	ALLOW correct answer if it follows an equation given in unit symbols IGNORE s.f. BUT must be correctly rounded from 6.4285...	1

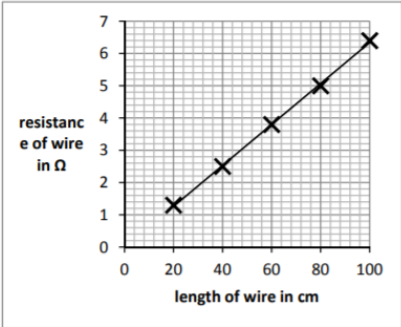Question Number	Answer	Notes	Marks										
(d) (i)	<p>Sample graph –</p>  <p>scale; at least half the paper axes labelled including units; Plotting; Plotting; Best fit line;</p>	<table border="1" data-bbox="927 286 1070 423"> <tr><td>20</td><td>1.3</td></tr> <tr><td>40</td><td>2.5</td></tr> <tr><td>60</td><td>3.8</td></tr> <tr><td>80</td><td>5.0</td></tr> <tr><td>100</td><td>(6.4)</td></tr> </table> <p>Points to plot</p> <p>IF AXES REVERSED, LOSE THE AXES MARK Ignore (100 cm, 6.4) ALLOW as length increases resistance increases ALLOW conclusions in terms of resistance per metre etc</p>	20	1.3	40	2.5	60	3.8	80	5.0	100	(6.4)	5
20	1.3												
40	2.5												
60	3.8												
80	5.0												
100	(6.4)												

Question Number	Answer	Notes	Marks
(d) (ii)	<p>MARK (ii) and (iii) together, credit points wherever seen (directly) proportional;</p>	<p>IGNORE 'as length increases current decreases' / conclusions relating to current</p>	1
MARK tog With			
(iii)	<p>any TWO of Straight line; Through (0,0); line slopes upwards; quoting appropriate values from the graph;</p>	<p>ALLOW constant gradient ALLOW positive correlation</p>	1
		Total	19

3.

Question number			Answer	Notes	Marks
3	(a)	(i)	power = voltage x current;	Accept rearrangements and symbols e.g. current = power ÷ voltage, $P=IV$, $I=P/V$ ignore a triangle mnemonic an eqn in units	1
		(ii)	2.9 (A);	Accept 2.92 (A), 2.916 (A)	1
	(b)	(i)	Any three of : MP1. if current gets too high/exceeds 13A or a set value; MP2. fuse (wire) melts / breaks; MP3. breaking circuit / switching off; MP4. prevents cable over heating;	allow: fuse blows stops current /flow of electrons	3
		(ii)	any one of: MP1. cable can't be fully extended; MP2. limits the use of the extension cable; MP3. can't exceed 1200 W; MP4. can't reach 10.0 (A) / max working value/eq; AND (because otherwise) 5 A fuse will blow/ will cut the power;	allow RA ignore vague comments re energy or power being too much or too high	2
		(iii)	(to prevent) the cable overheating/OWTTE;		1



Total 8 marks

4.

Question number	Answer	Notes	Marks
(a)	B (no earth connection);		1
(b)	C (the circuit cannot overheat if there is a fault);		1
(c)	A (in parallel);		1

Total 3 marks

5.

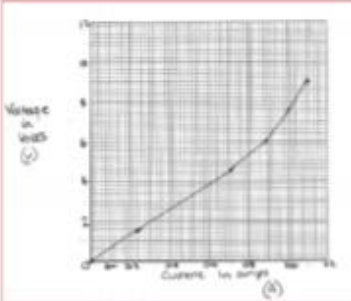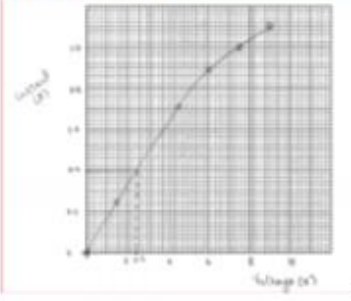Question number	Answer	Notes	Marks														
(a)	any 3 mistakes identified from MP1. cells are connected with wrong polarity; MP2. ammeter is connected in parallel (with wire); MP3. voltmeter is connected in series (with wire); MP4. circuit has not got a switch;	allow RA for any MP allow idea that meters should be swapped for two marks (MP2 and MP3)	3														
(b) (i)	suitable scale chosen (> 50% of grid used); axes labelled with quantities and unit; plotting correct to nearest half square (minus one for each plotting error) ;; line of best fit through zero;  = 4 not curve mark  = 5	only scales in 1,2,5,10 or 8 acceptable orientation unimportant points must be shown clearly i.e. two plotting errors = no marks for plotting i.e. smooth curve <table border="1" data-bbox="831 1032 979 1261"> <thead> <tr> <th>I</th> <th>V</th> </tr> </thead> <tbody> <tr> <td>0.0</td> <td>0.</td> </tr> <tr> <td>0.2</td> <td>1.</td> </tr> <tr> <td>0.7</td> <td>4.</td> </tr> <tr> <td>0.8</td> <td>6.</td> </tr> <tr> <td>1.0</td> <td>7.</td> </tr> <tr> <td>1.1</td> <td>9.</td> </tr> </tbody> </table>	I	V	0.0	0.	0.2	1.	0.7	4.	0.8	6.	1.0	7.	1.1	9.	5
I	V																
0.0	0.																
0.2	1.																
0.7	4.																
0.8	6.																
1.0	7.																
1.1	9.																
(ii)	0.40 A	range 0.39 A to 0.41 A	1														
(iii)	One of - MP1. Temperature (of wire) was not constant; MP2. Resistance (of wire) was not constant;		1														

Question number	Answer	Notes	Marks
(b) (iv)	Any four of - MP1. instrument to measure temperature; MP2. means to maintain constant temperature (of wire); MP3. use of $V = IR$; MP4. idea of repeating / averaging (at same temperature); MP5. idea of additional (interpolated) points; MP6. use linear part of the graph; MP7. use of gradient;	ignore all details about the circuit already given e.g. water bath, switch off and allow wire to cool $V \propto I$ obtain a range of values (of V, I) Allow reference to candidate's graph, e.g. current below 0.6 A Orientation unimportant	4

Total 14 marks