

Electricity Past Paper Answers WJEC Eduqas Physics A Level

1.

(a)	(i)	Electrons transferred from [polythene] rod to [metal cap] [or equiv] [Not just -ve charge]	1
	(ii)	+ve (1) because electrons [accept: negative charges] transferred from duster to rod (1).	2
(b)	(i)	Number of charged particles = $\frac{64 \times 10^{-9}}{1.6 \times 10^{-19}}$ (1) [Division by e ✓, answer ✓]	2
	(ii)	$I = \frac{Q}{t}$ or rearranged or $\frac{64 \times 10^{-9}}{2 \times 10^{-6}}$ (1) [or by impl.] $t = 32$ ms (1)	2
			[7]

2.

(a)		$V \propto I$ [or equiv. or in words] (1) provided that temperature remains constant (1)	2
(b)	(i)	Parallel sect: $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$ or $\frac{1}{80} + \frac{1}{80}$ or $R = \frac{R_1 R_2}{R_1 + R_2}$ or $\frac{80 \times 80}{80 + 80}$ (1) [or equiv or by impl.] $R_{\text{parallel}} = 40 \Omega$ (1) Total circuit resistance = 240Ω (1) [no e.c.f.]	3
	(ii)	I. $I = \frac{V}{R}$ or $\frac{9}{240 \text{ e.c.f.}}$ (1) = 37.5 mA (1) [Or potential divider approach with 7.5 V and 200Ω] II. 18.75 mA e.c.f.	2
	(iii)	Use of $P = I^2 R$ or $\frac{V^2}{R}$ or IV (1) P dissipated in A = $(37.5 \times 10^{-3})^2 \times 200 = 0.28$ W (1) e.c.f. P dissipated in C = $(18.75 \times 10^{-3})^2 \times 80 = 0.028$ W (1) e.c.f. $P_A : P_C = 10:1 \therefore$ A appears brighter. (1) [e.c.f. on a power attempt] [Bulb B instead of bulb A used -1]	4
			[12]

3.

(a)	Resistance of wire = 40 Ω	1
(b)	Temperature remains constant [or temperature change is (too) small (to affect resistance noticeably)] (1) Constant gradient → constant resistance [both parts needed] (1) [Accept: Voltage ∝ current <u>and</u> Ohm's Law obeyed] [Accept other well argued answer, e.g. wire could be constantan, which has negligible temperature variation of resistance, so graph doesn't tell us much.]	2
(c)	$\rho = \frac{RA}{l}$ [or by impl.](1) [i.e rearrangement of $R = \frac{\rho l}{A}$] $\rho = \frac{40 \text{ e.c.f.} \times \pi (1.0 \times 10^{-4})^2}{2.5}$ [Correct expression for area →(1)] $\rho = 5.0 \times 10^{-7} \Omega \text{ m}(1)$ ((unit))	3
(d)	Graph: Straight line graph through origin with lower gradient than original (1). With correct gradient [i.e. $\frac{1}{3}$ original] (1)	2
		[8]

4.

(a)	Flow of charge [acceptcharge/ions] or $\frac{[\Delta]Q}{[\Delta]t}$, if the symbols defined	1
(b)	(i) Sum of areas of triangle and rectangle areas attempted [or reasonable attempt at area of trapezium] (1) $Q = 3.0 \text{ C}$ ((unit))(1)	2
	(ii) No. of electrons = $\frac{3.0(\text{e.c.f.})}{1.6 \times 10^{-19}(1)} = 1.9 \times 10^{-19} (1)$ [1 st mark div by e]	2
	(iii) $I = 1.2(0) \text{ A}$ (from graph) (1); $v = \frac{I}{nAe}$ [manipulation shown – could be in following substitution – or by impl.](e.c.f. on I)(1) $= 3.75 \times 10^{-5} \text{ m s}^{-1}$ [accept $3.8 \times 10^{-5} \text{ m s}^{-1}$] (e.c.f. on I) (1)	3
		[8]

5.

(a)	Free [or equiv, e.g. conducting / moving / delocalised] electrons (1) collide / interact / hindered [by] (1) with atoms / ions of metal conductor / lattice ["particles" b.o.d.](1)	3
(b)	(i) I. [0 – 2 V]: Resistance constant / changes by v. small amount II. [2 – 8 V]: Resistance increases	1 1
	(ii) Either $R_{\text{bulb}} = \frac{6.0}{0.8(1)} = 7.5 \Omega (1)$ Total resistance = 5 Ω (1) [ecf] $\left[\text{Correct use of } \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \right]$ $I = 1.2 \text{ A} (1)$ [ecf on R]	Or $I \text{ through } 15\Omega = \frac{6.0}{15} (1) = 0.4 \text{ A} (1)$ $I \text{ through bulb} = 0.8 \text{ A} (1)$ $\therefore \text{Total current} = 1.2 \text{ A} (1)$
	(iii) Subst in $P = I^2 R$ [ecf on R and I] or in $P = \frac{V^2}{R}$ [ecf on R only] or $P = IV$ [ecf on I only] (1) $P = 7.2 \text{ W} (1)$	4 2 [11]

6.

(a)	(i)	Wire with rule positioned (1) and <u>labelled</u> moving pointer / jockey / croc clip (1) Either correctly positioned ohm-meter with no power supply or correctly position ammeter and voltmeter with power supply (1)	3			
	(ii)	[Different] length[s] of wire (1) Either measure V and I or measure / read R (1)		2		
	(iii)	Diameter of wire [not radius or csa by accept “thickness”] with micrometer / vernier calliper		1		
	(iv)	cross-sectional area fro πr^2 or $\pi(d/2)^2$ (1) graph of R against l [or mean value of R/l] (1) $\rho = \text{gradient} \times [\text{cs}]a$ [or mean value of $R/l \times \text{csa}$] (1) [NB $R = V/I$ given here can be used to credit 2 nd mark of (ii)] [NB Finding R for a measured length and [cs] area and then ρ calculated \rightarrow 1 only]		3		
	(b)	(i)		$R \propto l$ (1) $\therefore R$ <u>increases</u> as strain gauge gets longer (1) $R \propto 1/A$ (1) $\therefore R$ <u>increases</u> as the strain gauge gets thinner (1) [or $R = \frac{\rho l}{A}$ or $\rho = \frac{RA}{l}$ (1), A increases & l decreases (1) ρ doesn't change /constant (1) so resistance increases (1)]	4	
	(ii)	[csa =] $0.2 \times 10^{-3} \times 0.0012 \times 10^{-3}$ [or equiv.] (1) $\rho = 4.9 \times 10^{-7} \Omega \text{ m}$ ((unit)) (1) [ecf from csa calculation] [ecf on powers of 10 in both A and l]		2		
	(iii)	<table border="0" style="width: 100%;"> <tr> <td style="width: 50%; vertical-align: top;"> Either $1.6 = \frac{650}{650 + R} \times 6$ (1) Manipulation (1); $R = 1788 \Omega$ (1) </td> <td style="width: 50%; vertical-align: top;"> Or $I = \frac{1.6}{650} (=2.46 \times 10^{-3} \text{ A})$ (1) $R = \frac{(6 - 1.6)(1)}{2.46 \times 10^{-3}} = 1788 \Omega$ (1) </td> </tr> </table>		Either $1.6 = \frac{650}{650 + R} \times 6$ (1) Manipulation (1); $R = 1788 \Omega$ (1)	Or $I = \frac{1.6}{650} (=2.46 \times 10^{-3} \text{ A})$ (1) $R = \frac{(6 - 1.6)(1)}{2.46 \times 10^{-3}} = 1788 \Omega$ (1)	3
	Either $1.6 = \frac{650}{650 + R} \times 6$ (1) Manipulation (1); $R = 1788 \Omega$ (1)	Or $I = \frac{1.6}{650} (=2.46 \times 10^{-3} \text{ A})$ (1) $R = \frac{(6 - 1.6)(1)}{2.46 \times 10^{-3}} = 1788 \Omega$ (1)				
	[18]					

7.

(a)	(i)	[For a metallic conductor] the potential difference and current are [directly] proportional/ $I \propto V$ (1), provided the temperature remains constant / all physical factors remain constant (1) V = IR only no marks	2
	(ii)	It is constant / stays the same / increases as the temperature increases	1
(b)	(i)	$A = 1.5(3) \times 10^{-8} \text{ [m}^2\text{]}(1)$ $R = \frac{\rho l}{A} = \frac{95 \times 10^{-8} \times 3.2}{1.5(3) \times 10^{-8}}(1) = 199 \text{ [}\Omega\text{]}(1)$	3
	(ii)	$\frac{230^2}{200} = 265 \text{ [W]}$ allow e.c.f. from (b)(i)	1
	(iii)	$\frac{1}{66.7(1)} = \frac{1}{200} + \frac{1}{R_2}(1)$ $R_2 = 100 \text{ [}\Omega\text{]}(1)$	3
	(iv)	R_2 (1) either reference to $\frac{V^2}{R}$ so lower R / same V across lower R or reference to $I^2 R$ so greater I or reference to IV so I increased [for constant V] or correct calculation of R_2 (1)	2
	(v)	$\frac{230}{66.7} = 3.5 \text{ [A]}$ allow e.c.f. from (b)(iii)	1
Question 1 total			[13]


8.

(a)	(i)	Diagram to include <ul style="list-style-type: none"> • Correct electric circuit with ohmmeter or power supply with ammeter + voltmeter with correct symbols and positioning (1) • Method of heating shown (1) • Method of recording temperature shown (1) 	3
	(ii)	Linear [or approximately linear] graph with positive gradient (1) and positive intercept on R axis (1).	2
(b)	(i)	Conducting / delocalised / free electrons (1) collide (1) with metal lattice / atoms / ions (1) [not with other free electrons]	3
	(ii)	The greater the temperature the greater the vibrational energy of the lattice / metal ions (1) producing a greater chance [or rate] of collisions/ collisions more often / greater frequency of collisions (1) [not harder] .	2
Question 2 total			[10]

9.

(a)	(i)	Electron	1
	(ii)	Negative charges repelled [by rod] (1) and move from A to B/ to the right (1) leaving A with a net positive charge (1)	3
	(iii)	Diagram with A shown as positive and B as negative (1) and the charges shown on the sides of the sphere which are nearly touching.(1)	2
(b)	(i)	$[1.6 \times 10^{-19} \times 300 \times 10^9 =] 4.8 \times 10^{-8} \text{ C UNIT mark}$	1
	(ii)	$I = \frac{4.8 \times 10^{-8}}{20 \times 10^{-12}} (1) = 2.4 \times 10^3 \text{ [A]} (1)$ allow e.c.f from (b)(i)	2
Question 5 Total			[9]

10.

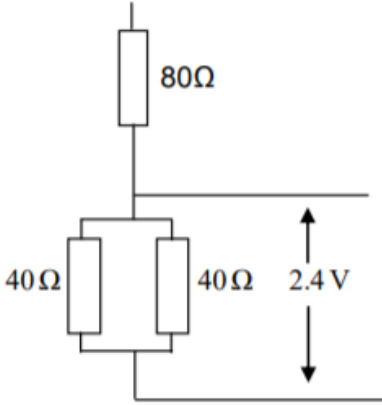(a)	(i)	$Resistance = \frac{pd}{current}$ (accept: voltage / if V and I written must be qualified)	[1]
	(ii)	$V = JC^{-1} (1); I = C s^{-1} (1);$ Convincing working (1) Don't accept use of t -award ecf for 3 rd mark. Alternative route using power formulae is acceptable.	[3]
(b)	(i)	$I = \frac{V_{in}}{R_1 + R_2}$	[1]
	(ii)	$V_{out} = IR_2 (1); I$ (from (i)) used correctly (1)	[2]
(c)	(i)	Any parallel combination shown (1); $40 [\Omega]$ used correctly (1)	[2]
	(ii)	 <p>Resistor combination shown (1) ecf from (c)(i)</p> <p>2.4[V] or V_{out} labelled correctly (1)</p>	[2]
Question 2 total			[11]

11.

<p>(a)</p> <p>(b)</p>	<p>(i) Point where entire weight of object acts. Don't accept mass.</p> <p>(ii) $\tan \theta = 40/60$ (1); $\theta = 33.7^\circ$ (1)</p> <p>(i) $V = 0.6 \times 0.4 \times 0.1$ (1); $M = \rho \times V$ used correctly (1)</p> <p>(ii) $T \sin \theta$ or equivalent (1) $\times 1.2$ (1) = $9.6 \times 9.81 \times 1.8$ (1)</p> <p>$T = 220$ [N] (1)</p> <p>(iii) $F = 220$ (ecf) $\cos 40^\circ$ or equivalent (1)</p> <p>$F = 169$ [N] (1)</p> <p>Accept Pythagoras solution.</p> <p>Question 5 Total</p>	<p>[1]</p> <p>[2]</p> <p>[2]</p> <p>[4]</p> <p>[2]</p> <p>[11]</p>
<p>(a)</p> <p>(b)</p>	<p>(i) Correct and convincing use of $\rho = \frac{RA}{l}$ (including unit conversion)</p> <p>(ii) $\left(\frac{2000}{11.2}\right) = 179$ A unit mark</p> <p>(iii) $v = \frac{I}{nAe}$ rearranged (or shown numerically) (1)</p> <p>$n = 6.0 \times 10^{28} \times 3$ (1)</p> <p>$v = 1.55 \times 10^{-5}$ [ms⁻¹] (ecf on I and n) (1)</p> <p>(i) Same (or equivalent)</p> <p>(ii) v increased (1) because...; A decreased, I, n, e unchanged by implication (1)</p> <p>(iii) Increased frequency / more collisions between electrons and lattice / atoms / ions or electrons carry greater kinetic energy (1) leading to increased vibrational / kinetic energy of lattice atoms (1)</p> <p>Question 6 Total</p>	<p>[1]</p> <p>[1]</p> <p>[3]</p> <p>[1]</p> <p>[2]</p> <p>[2]</p> <p>[10]</p>