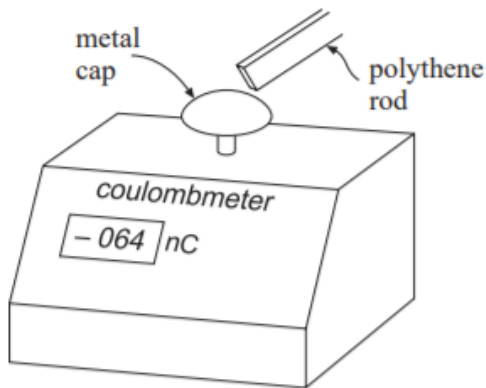


Electricity Past Paper Questions WJEC Eduqas Physics A Level

1.

A polythene rod is rubbed with a duster. The rod is then scraped across the metal cap of a digital coulombmeter as shown in the diagram (a coulombmeter is a device for measuring electrical charge).



(a) (i) Explain why the reading on the coulombmeter is negative. [1]

.....

.....

.....

.....

(ii) State the sign of the charge acquired by the duster. Explain your reasoning. [2]

.....

.....

.....

(b) The coulombmeter is now discharged by connecting a wire from the metal cap to the ground. The coulombmeter reading falls to zero.

(i) Calculate the number of charged particles that flow from the coulombmeter. [2]

.....

.....

.....

(ii) Calculate the time taken for this number of charged particles to flow past a point in the wire if the mean discharge current is $2 \mu\text{A}$. [2]

.....

.....


2.

(a) State Ohm's law. [2]

.....

.....

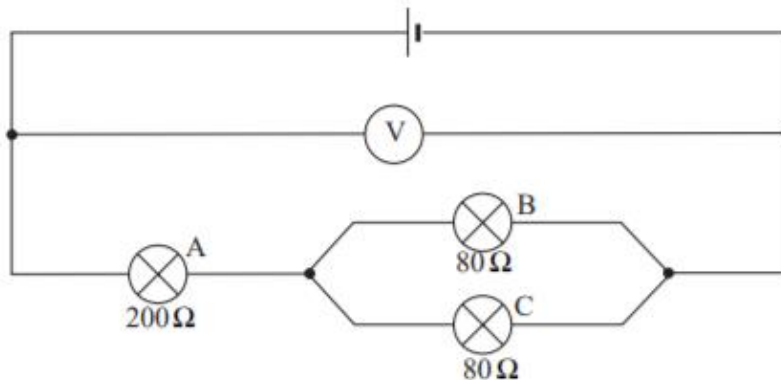(b) In the circuit below the voltmeter reads 9 V and the resistance of the bulbs are as shown.



(i) Calculate the effective resistance of the bulb combination. [3]

.....

.....

.....

(ii) Calculate the current through

(I) bulb A; [2]

.....

.....

(II) bulb C. [1]

.....

(iii) Calculate the ratio of the power dissipated in bulbs A and C and compare the brightness of the bulbs. [4]

.....


.....

.....

.....

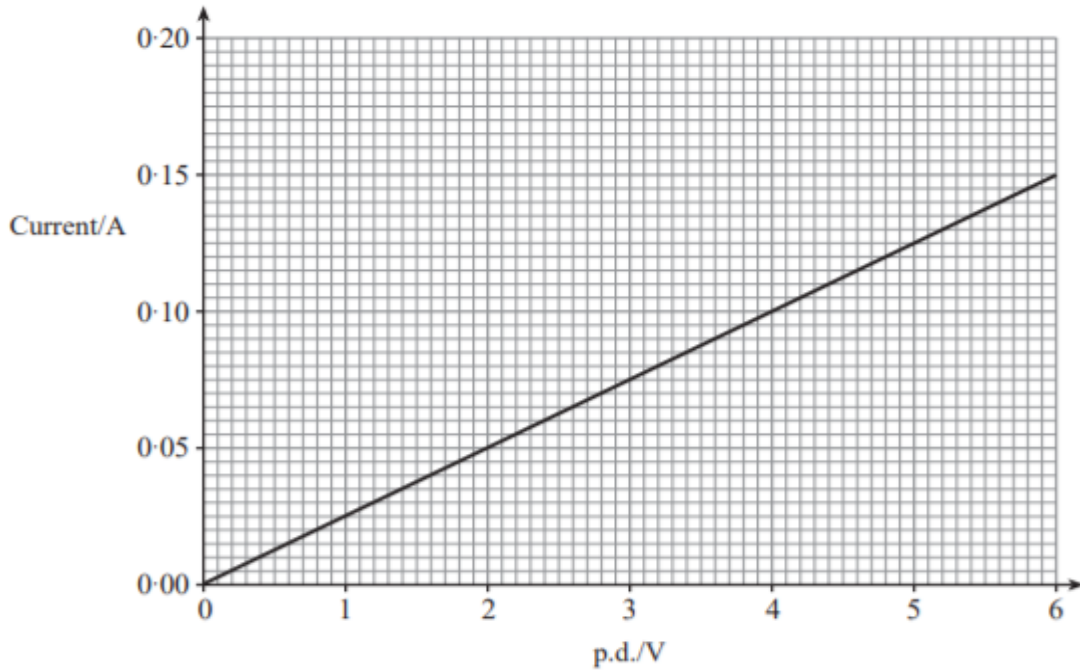3.

A graph of current against potential difference (p.d.) is given for a piece of metal wire.



(a) Calculate the resistance of the wire. [1]

.....

.....

(b) What does the graph tell us about the temperature of the wire as the p.d. across it is increased? Explain your answer. [2]

.....

.....

.....

(c) The wire has a length of 2.5 m and a **diameter** of 2.0×10^{-4} m. Calculate the resistivity of the metal. [3]

.....

.....

.....

.....

(d) Draw on the same graph-grid the current against p.d. graph for a wire, made of the same metal and of the same diameter (2.0×10^{-4} m) but of length 7.5 m. [2]

4.


1. (a) Explain what is meant by an electric current. [1]

.....

.....

- (b) The current through a conductor changes with time over a period of 3.0 s as shown.

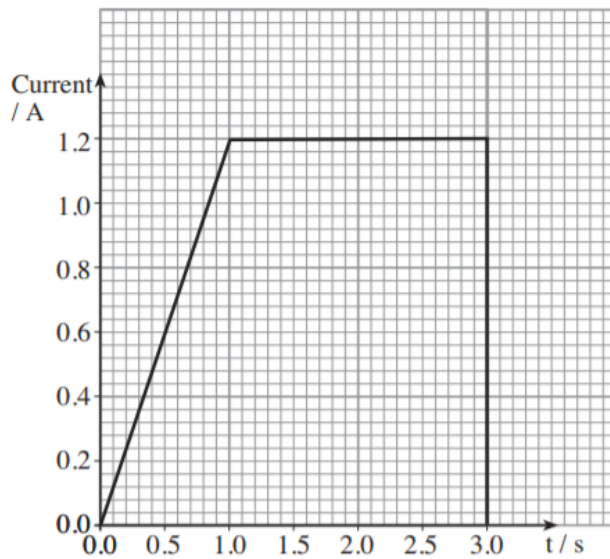- (i) By considering the area under the graph calculate the total charge passing through the conductor in this time. [2]



.....

.....

.....

- (ii) Calculate the total number of electrons flowing past a point in the conductor in this time. [2]

.....

.....

.....

- (iii) Calculate the drift velocity of the electrons at $t = 1.5$ s. Take the cross-sectional area of the conductor to be $2.0 \times 10^{-6} \text{ m}^2$ and the number of free electrons per m^3 to be $1.0 \times 10^{29} \text{ m}^{-3}$. [3]

.....

.....

5.

(a) Explain how electrical resistance arises in metal conductors.


[3]

.....

.....

.....

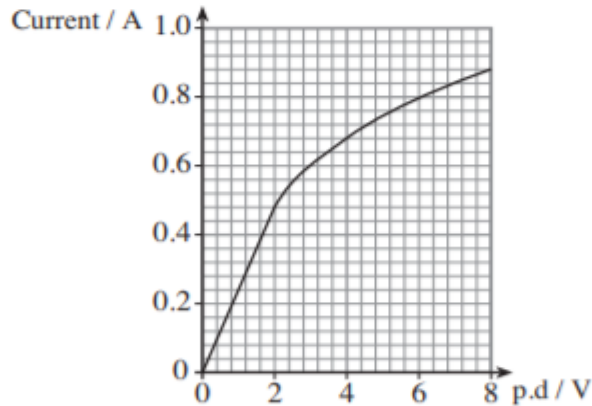(b) A current-voltage graph for a filament lamp is shown.



(i) Describe how the **resistance** of the lamp changes as the voltage across it increases over the range

(I) 0 V – 2 V;

[1]

.....


(II) 2 V – 8 V.

[1]

.....

(ii) The lamp is connected in parallel to a 15Ω resistor and to a 6 V supply as shown. Calculate the current through the ammeter.

[4]

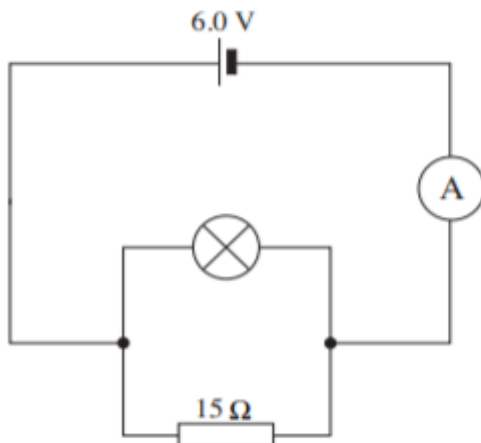

.....

.....

.....

.....

.....

(iii) Calculate the power dissipated in the circuit.

[2]

.....

.....

6.

(a) (i) Draw a labelled diagram of the apparatus you could use to determine the relationship between the resistance and length of a wire. [3]

(ii) State what measurements you need to make. [2]

.....

.....

.....

(iii) What further measurement would you need to make to determine the resistivity of the metal and what apparatus would you use to make this measurement? [1]

.....

(iv) Explain how a value of the resistivity is determined from your measurements. [3]

.....


.....

.....

.....

.....

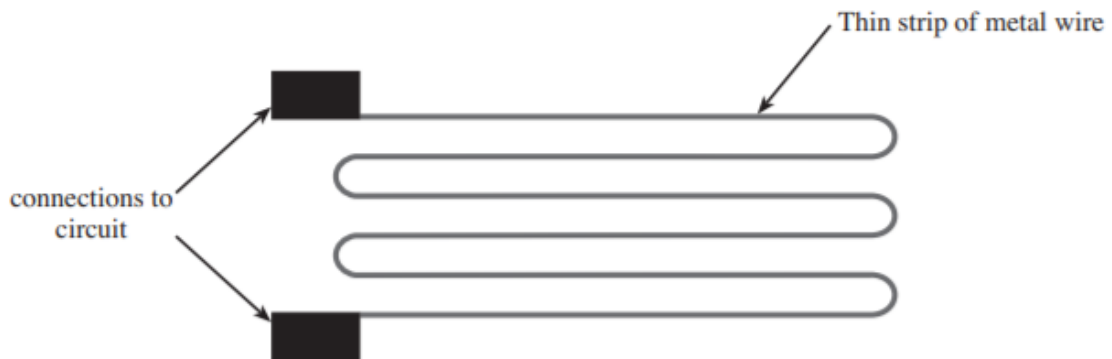- (b) A strain gauge is a device used to monitor distortions in structures such as bridges and buildings. It consists of a thin strip of metal wire as shown which is then attached to the structure under test.



- (i) When the structure extends, the wire in the strain gauge gets **thinner** and **longer** thus changing its resistance. Using the resistivity equation explain whether the resistance of the strain gauge increases or decreases when the structure extends. [4]

.....

.....


.....

.....

.....

.....

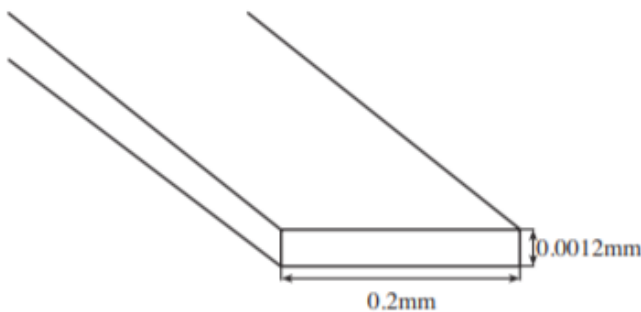- (ii) Calculate the resistivity of the metal in a strain gauge which has a resistance of 650Ω and a total length of 32 cm. The thin metal strip is 0.2 mm wide and 0.0012 mm thick as shown. [2]



Thin metal strip (magnified - not to scale)

.....

.....


.....

.....

.....

.....

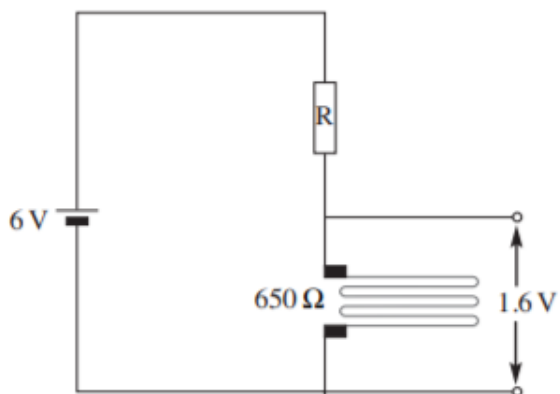- (iii) The changing resistance of a strain gauge is monitored using a potential divider circuit. The gauge is placed in series with a fixed resistor R as shown. Calculate the value of R which will give a p.d. of 1.6V across the strain gauge. [3]



.....

.....

.....

.....

.....

.....

.....

.....

7.

- (a) (i) State Ohm's law. [2]

.....


.....

.....

- (ii) What can be said about the resistance of a conductor that obeys Ohm's law? [1]

.....

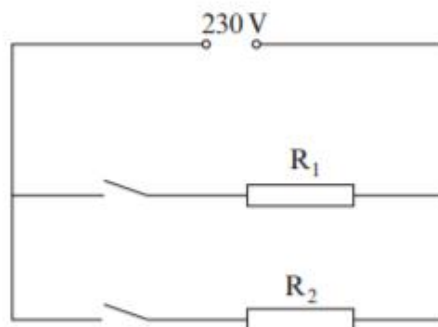- (b) The heating circuit of a hairdryer consists of two heating elements R_1 and R_2 connected in parallel as shown. The elements are made from wire of the same material of resistivity $95 \times 10^{-8} \Omega\text{m}$ and diameter $1.4 \times 10^{-4}\text{m}$.



- (i) The length of wire used to make R_1 is 3.2m. Show that the resistance of R_1 is approximately 200Ω . [3]

.....

.....

.....

- (ii) Calculate the power output from the heating circuit with only R_1 switched on. [1]

.....

.....

- (iii) With both elements switched on the **total resistance** is only a third of the resistance of R_1 on its own. Calculate the resistance of R_2 . [3]

.....

.....

.....

- (iv) Explain which element, R_1 or R_2 , would provide the greater power output from the heating circuit. [2]

.....

.....

.....

- (v) Calculate the total current with both elements switched on. [1]


.....

.....

8.

- (a) (i) Draw a labelled diagram of the apparatus you would use to determine the relationship between the resistance and temperature of a metal wire. [3]

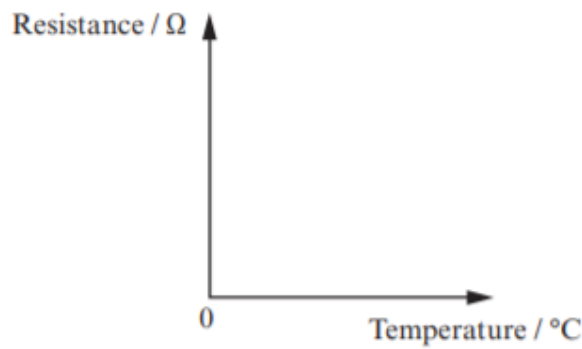- (ii) Sketch, on the axis below, a graph of the results you would expect from the experiment. [2]



- (b) (i) Explain in terms of particles how electrical resistance arises in metal conductors. [3]

.....

.....

.....

.....

.....


- (ii) Hence suggest an explanation for your results to the experiment in part (a). [2]

.....

.....

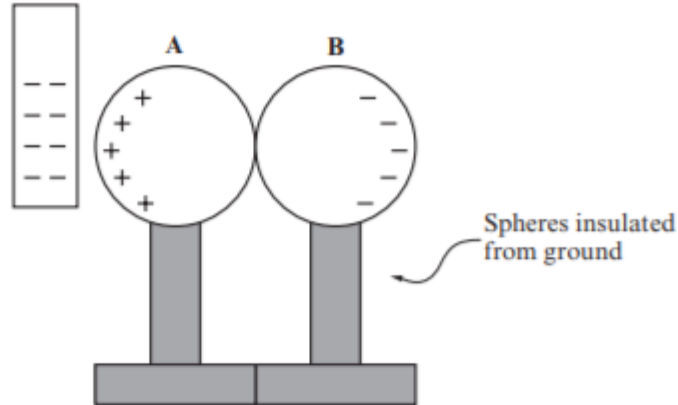9.

Two insulated metal spheres, **A** and **B** are placed in contact with each other. When a negatively charged rod is brought near, the charges become distributed on the metal spheres as shown.



(a) (i) State the particle which carries the negative charge. [1]

(ii) Explain why the charges become distributed as shown. [3]

.....

.....

.....

.....


.....

.....

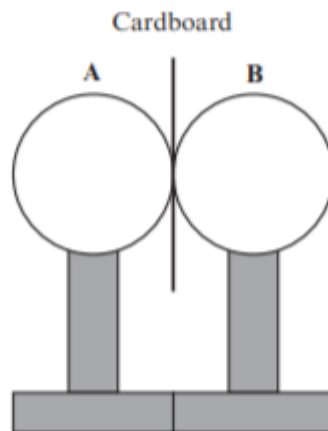(iii) The following procedure is carried out:

- A thin insulating piece of cardboard is placed in between the spheres.
- The negatively charged rod is then removed.

Sketch the distribution of charges now on both spheres. [2]



- (b) (i) In another process, a negatively charged rod is rubbed against one of the spheres and in doing so places approximately 300×10^9 free negative charges onto the sphere. Calculate the charge on the sphere. [1]

.....

.....

.....

- (ii) The sphere is discharged in a time of 20 ps by connecting a wire from it to the ground. Calculate the mean current. [2]

.....

.....

.....

.....

10.

(a) (i) Define resistance.

[1]

.....

.....

(ii) The unit of resistance is the ohm (Ω). Show that it is possible to express the Ω as

[3]

$$\text{J s C}^{-2}$$


.....

.....

.....

.....

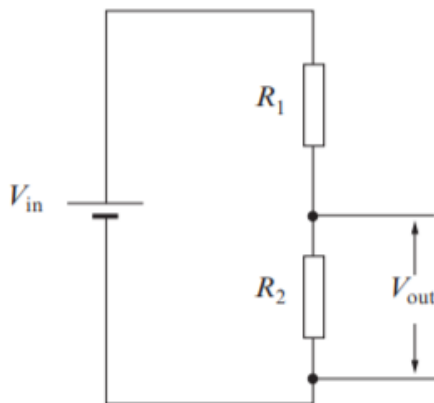(b) The diagram shows a potential divider.



(i) Write down an equation for the current through resistors R_1 and R_2 when the input pd V_{in} is applied as shown. [1]

.....

.....

.....

(ii) Hence show that the output pd V_{out} is given by the equation [2]

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$

.....


.....

.....

(c) Three resistors are available with values $40\ \Omega$, $40\ \Omega$ and $80\ \Omega$.

(i) Draw a diagram showing how **two** of these resistors can be connected together to give a combined resistance of $20\ \Omega$. [2]

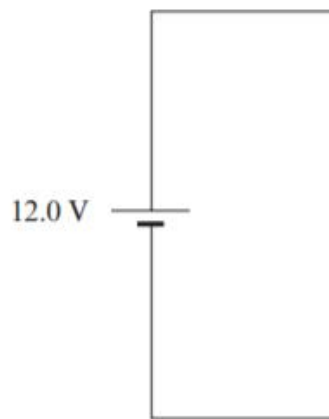(ii) Hence, using all three of the resistors, complete the following potential divider circuit for which $V_{\text{out}} = 2.4\ \text{V}$ when $V_{\text{in}} = 12.0\ \text{V}$. Clearly label the resistor values and V_{out} on your diagram. [2]



11.

A power cable has a resistance of 11.2Ω and is made of an alloy of aluminium of resistivity $2.8 \times 10^{-8}\Omega\text{m}$. It is used to link a power station to a town 160 km away.

- (a) (i) Show that the cross-sectional area of the cable is $4.0 \times 10^{-4}\text{m}^2$. [1]

.....

.....

- (ii) Calculate the current in the cable given that the pd across it is 2.0 kV. [1]

.....


- (iii) Calculate the mean drift velocity of the free electrons in the cable given that there are 6.0×10^{28} atoms per m^3 of aluminium and each atom contributes 3 free electrons. [3]

.....

.....

.....

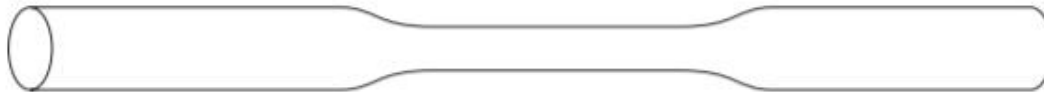- (b) A small portion of the cable is damaged. As a result its cross-sectional area is less than that of the rest of the cable, as shown in the diagram.



- (i) State how the current in the thinner portion compares with the current in the rest of the cable. [1]

.....

- (ii) State how the mean drift velocity of free electrons in the thinner portion compares with that in the rest of the cable. Justify your answer. [2]

.....

.....

.....

- (iii) Hence suggest, in terms of particles, why the damaged part of the cable will be prone to overheating. [2]

.....

.....