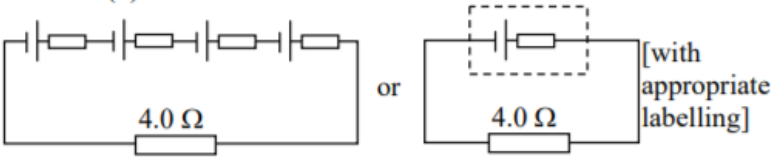


Internal Resistance of Cells Answers WJEC Physics A Level

1.

(a)	<p>'per unit charge' [or 'per coulomb'] used correctly at least once. (1) V = energy delivered [per unit charge] to [external] circuit (1) E = energy supplied [per unit charge] from chemical energy of cell (1) Ir = energy wasted / lost / dissipated [per coulomb] in the internal resistance (1)</p>	4
(b)	<p>(i)  [with appropriate labelling]</p> <p>[or equivalent]</p> <p>(ii) $R_{\text{Total}} = 4.8 \Omega$ [or by impl.] (1) $I = 1.25 \text{ A}$ (1) [Accept 1.3 A] no e.c.f.</p> <p>(iii) P.d. across 4Ω resistor = 5.0 V [e.c.f. $4.0 \times (b)(i)$ ans]</p>	1
(c)	<p>5.7V and $R_{\text{tot}} = 5.0 \Omega$ (with) or 4.5V and $R_{\text{tot}} = 4.6 \Omega$ (without cell)(1) With run-down cell: $I = 1.14 \text{ A}$ (1) Without run-down cell: $I = 0.98 \text{ A}$ (1) Conclusion: better not to remove (e.c.f.); strategy + conclusion (1)</p>	4 [12]

2.

Question	Marking details	Marks Available
(a)	The electrical (potential) <u>energy transferred</u> [or <u>work done</u>] <i>per coulomb / unit charge passing through the cell</i> [<u>Underlined</u> (1); <i>italic</i> (1)]	2
(b)	Voltmeter shown in parallel with cell [outside the dotted line – accept inside the line if outside the cell/i.r combination] [Accept equivalent, e.g. connected in parallel with resistor]	1
(c)	All points correctly plotted (2) [-1 per mistake, min 0] Line correctly drawn [with extrapolation just to V axis] (1)	3
(d)	(i) [e.m.f. =] 1.6 V	1
	(ii) gradient attempted [or by impl.](1); $r = 0.33 \Omega / 0.3 \Omega / \frac{1}{3} \Omega$ (1)	2
		[10]

3.

Question	Marking details	Marks Available
(a)	<p>V- energy (per coulomb) used in [external] resistor / circuit. (1) E- energy (per coulomb) transferred / supplied by source / in the whole circuit (1) Ir- energy (per coulomb) wasted / lost in source / cell / internal resistance (1) Use of 'per coulomb / unit charge' once. (1)</p>	[4]
(b)	<p>(i) $4[\Omega]$ (1) (ii) Gradient attempted e.g. 60/10 (1) (or use of equation ecf from (b) (i)) $\text{emf} = 6[\text{V}]$ (1) (iii) $1/I = 4[\text{A}^{-1}]$ or by implication (1) $R = 20[\Omega]$ (1) Use of I^2R i.e. $(0.25)^2 \times 20$ (ecf) (1) or correct substitution into both $V = IR$ and $P = IV$ or V^2/R $P = 1.25[\text{W}]$ (1)</p>	[1] [2] [4]
(c)	<p>(i) $\text{emf} = 12.0[\text{V}]$ (ecf) and $r = 8.0[\Omega]$ (ecf) (ii) $R = 52.0[\Omega]$ (ecf) (iii) y intercept ($r \rightarrow 8.0\Omega$ (ecf)) (1) Precise gradient e.g. through (5,52) (ecf) (1)</p>	[1] [1] [2]
	Question 7 Total	[15]

4.

Question	Marking details	Marks Available
(a)	(i) V is the terminal p.d. – or clear explanation in energy terms: energy per coulomb delivered to <u>external circuit</u> / [NB “per coulomb” / “per unit charge” required on one of (i) and (ii) if energy explanation given] (ii) P.D. across the internal resistance [accept lost volts – “bod”] / energy per coulomb lost / dissipated in the internal resistance / cell	1 1
(b)	(i) 2.4 V (ii) 0.4Ω [allow e.c.f. from (b)(i)] (iii) e.g. “Drains” the cell <u>quickly</u> , Cell gets hot	1 1 1
(c)	Correct use of $I = \frac{E}{R_{\text{Tot}}}$ $I = 1.0 \text{ A}$	2
(d)	Trial and error acceptable: Use of $1 \times, 2 \times, 3 \times \dots$ (1); corresponding total resistance (1); use of $\frac{V}{R}$ (1) leading to 5 cells (1) Nice answer: Subst in $I = \frac{E}{R+r} : 3.0 = \frac{2.4n}{2.0+0.4n}$ [ecf on $n \times 2$](1) Re-arrangement: $6.0 + 1.2n = 2.4n \rightarrow n = 5$ Marking points with analytical answer: $n \times 2.4$ (1) Use of total resistance = $2.0 + 0.4 n$ (1) Application of $I = \frac{V}{R}$ (1); $n = 5$ (1)	4 [11]

5.

Question	Marking details	Marks Available
(a)	(i) <u>12</u> Joules per coulomb (1) Supplied from cell / source / battery / chemical to electrical (1)	2
	(ii) Energy lost in the resistance of cell	1
(b)	$\left\{ \frac{3.6(1)}{120} \right\} = 0.03 \text{ } [\Omega] \text{ (1)}$	2
(c)	$I = \frac{12}{0.03} = 400 \text{ [A]}$ ecf from (b)	1
(d)	(i) $Q = 3 \times [(16 \times 60^2) \text{ or } 57\,600 \text{ (1)}]$ $= 172800 \text{ [C] (1)}$	2
	(ii) $t = \frac{172,800}{120} = 1440 \text{ seconds / 24 mins UNIT mark}$ Allow ecf from (d) (i)	1
	Question 3 Total	[9]

6.

Question	Marking details	Marks Available
(a)	[Electrical] energy [or work done] transferred to whole of circuit [or through cell] (1) per coulomb [or unit charge] (1)	[2]
(b)	Sensible scale and axes labelled with units (1) All points correct $\pm \frac{1}{2}$ small square division (1) Line of best fit (1) (no requirement \rightarrow y axis)	[3]
(c)	(i) $E = 1.48 \text{ [V]} (\pm 0.01 \text{ V})$ ecf from graph	[1]
	(ii) Gradient attempted or $r = \frac{E - V}{I}$ (by implication) (1) $r = 0.83 \text{ } [\Omega] \text{ (1) ecf from graph}$	[2]
(d)	$I = \frac{E}{R + r} \left\{ \frac{1.48}{6 + 0.83} \right\} \text{ (1) (ecf on } E \text{ and } r) \quad I = 0.22 \text{ A (1)}$ $t = 20 \times 60 \text{ [1 200 s] (1)}$ $Q = 0.22 \text{ (ecf)} \times 1\,200 \text{ (ecf)} = 264 \text{ [C] (1)}$	[4]
	Question 3 Total	[12]

7.

Question	Marking details	marks Available
(a)	(i) Diagram A: Current through X less than current through Y (or vice-versa) pd across X same as than pd across Y [Both statements correct for 1 mark]	[1]
	(ii) Diagram B: Current through X same as current through Y pd across X greater than pd across Y [Both statements correct for 1 mark]	[1]
(b)	(i) Resistance has decreased by factor 1.5 (or reduced to 2/3 original value) or other correct quantitative comparison. Do not accept reduced by $4\ \Omega$ (1) Therefore current increases by same factor (or $\times 1.5$) etc. (1) Accept answers based on calculation: V across $12.0\ \Omega = 2.4\ [V]$ (1) I through $8.0\ \Omega = \frac{2.4}{8.0} (= 0.3\ A)$ (1)	[2]
	(ii) Current = $0.5\ [A]$ (1) Total resistance = $10.8\ [\Omega]$ (1) 0.5×10.8 seen (1) Alternative – pd across parallel combination = $0.2 \times 12 = 2.4\ [V]$ (1) pd across $6.0\ \Omega = (0.2 + 0.3) \times 6 = 3.0\ [V]$ (1) Total $pd = 2.4 + 3.0$ (1) = $[5.4\ V]$	[3]
	(iii) Some voltage (accept energy) is lost/ given out as heat (1) in the internal resistance of the cell (1)	[2]
	(iv) Substitution into $E = V + Ir$ (e.g. $r = \frac{6 - 5.4}{0.5}$) (1) $r = 1.2\ [\Omega]$ (1) deduct 1 mark for incorrect sign	[2]
	Question 5 Total	[11]