

Internal Resistance of Cells Questions WJEC Physics A Level

1.

An equation which can be applied to a circuit containing a cell of e.m.f. E and internal resistance r is

$$V = E - Ir$$

- (a) Explain carefully, **in terms of energy**, the meanings of V , E and Ir . [4]

.....

.....

.....

.....

.....

.....

.....

.....

.....

- (b) Four cells, each of e.m.f. 1.5 V and internal resistance $0.2\ \Omega$, are connected in series to make a battery of e.m.f. 6.0 V . A $4.0\ \Omega$ resistor is connected across the battery.

- (i) Draw a circuit diagram of this arrangement which includes the internal resistance of the battery. [1]

- (ii) Calculate the current. [2]

.....

.....

.....

- (iii) Calculate the p.d. across the $4.0\ \Omega$ resistor. [1]

.....

.....

- (c) After the resistor has been left connected for some time, one of the cells starts to show signs of running down. Its e.m.f. has dropped to 1.20 V and its internal resistance has risen to $0.40\ \Omega$. Investigate whether or not, in order to maximise the current through the $4.0\ \Omega$ resistor, it would be better to remove the run down cell, leaving the other three in series. [4]


2.

(a) Define the *e.m.f.* of a cell. [2]

.....


.....

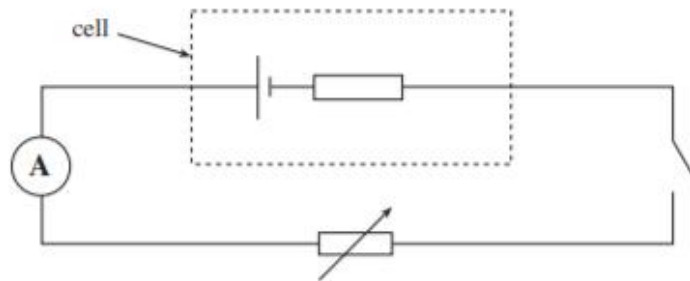(b) A student sets up the following circuit to find the e.m.f. and internal resistance of a cell. Complete the circuit diagram by adding a voltmeter. [1]



(c) With the circuit complete the student obtains the following results. Plot these results on the grid and draw a line through your points. [3]

| p.d. across cell terminals /V | Current /A |
|-------------------------------|------------|
| 1.4 | 0.6 |
| 1.2 | 1.2 |
| 1.0 | 1.8 |
| 0.8 | 2.4 |
| 0.6 | 3.0 |

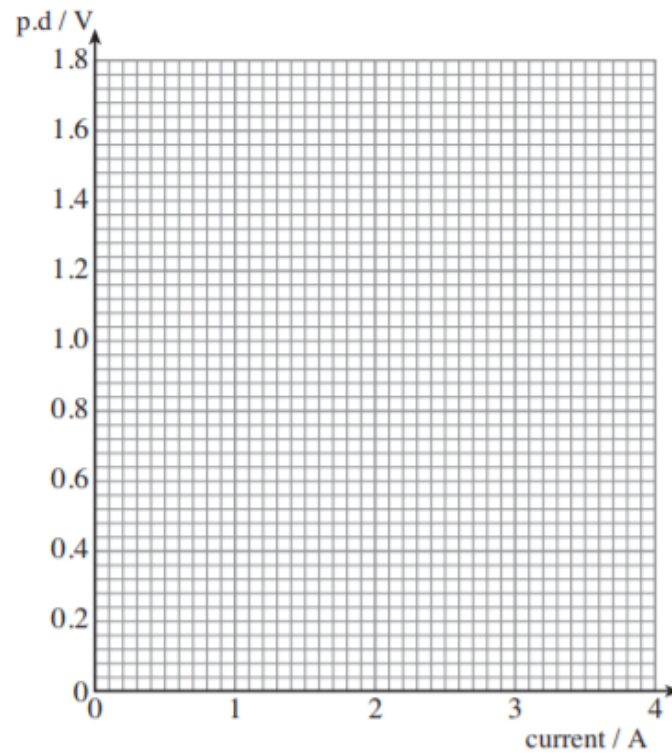

(d) Use your graph to determine

(i) the e.m.f of the cell; [1]

.....

(ii) the internal resistance of the cell. [2]


.....

.....

.....

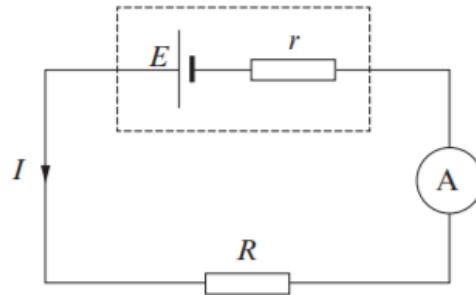3.

A student sets up the following circuit using a cell of emf E and internal resistance r .



(a) An equation which can be applied to the above circuit is

$$V = E - Ir$$

Explain, **in terms of energy**, the meanings of V , E and Ir .

[4]

.....

.....

.....

.....

.....


.....

.....

.....

.....

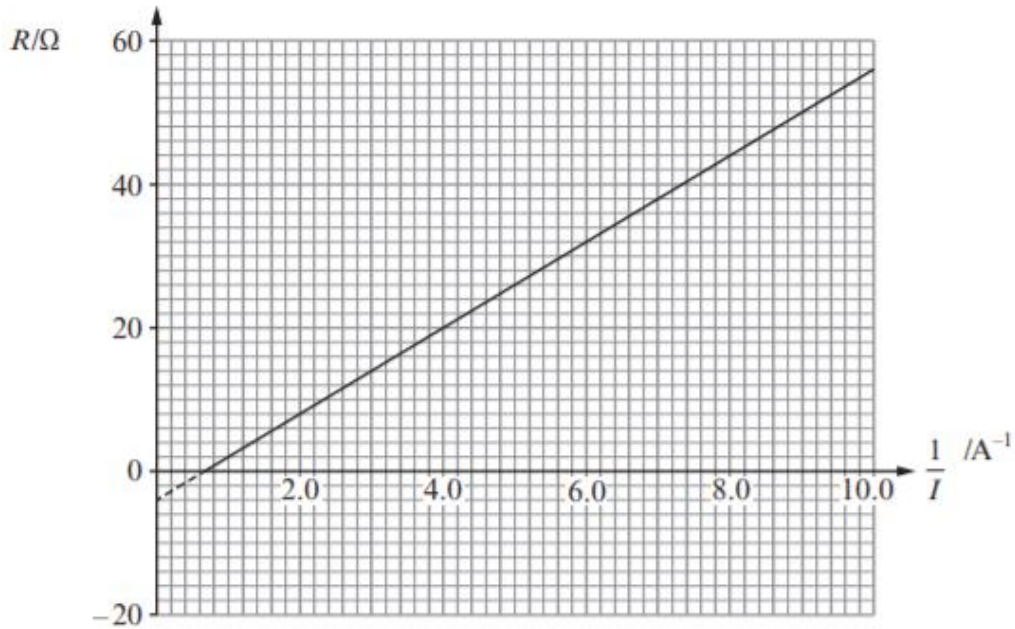- (b) The student measures the current I for different values of R . She then plots a graph of R against $\frac{1}{I}$.



The equation for this graph is

$$R = \frac{E}{I} - r$$

- (i) Use the graph to find the internal resistance, r , of the cell. [1]
-
- (ii) Determine the emf of the cell. [2]
-
-
-
- (iii) Referring to the graph, calculate the power dissipated in the resistor R when there is a current of 0.25 A. [4]
-
-
-
-
-

4.

(a) An equation which can be applied to a cell of emf E and internal resistance r is

$$V = E - Ir$$

(i) What does V represent? [1]

.....



.....

(ii) What does Ir represent? [1]

.....

.....

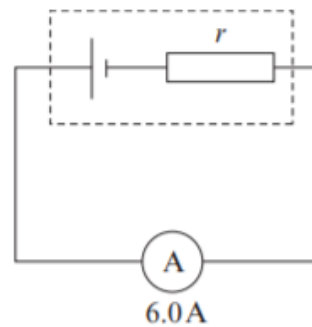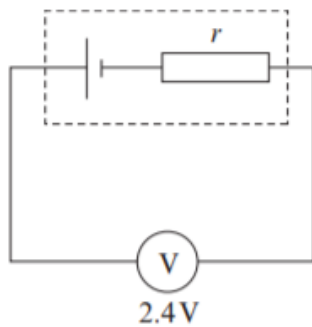(b) A voltmeter connected across the terminals of a cell reads 2.4 V. An ammeter (whose resistance is zero) reads 6.0 A when connected briefly across the cell.



(i) Write down the emf of the cell. [1]

(ii) Calculate the internal resistance of the cell. [1]

.....


.....

(iii) Give one reason for not leaving the ammeter connected to the cell. [1]

.....

.....

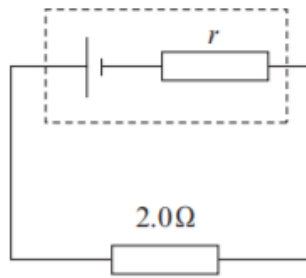- (c) Calculate the current through a 2.0Ω resistor when it is connected across the cell. [2]



.....

.....

.....

- (d) Determine the number of cells of this type which, when connected in series with the 2.0Ω resistor, will produce a current of 3.0 A . [4]

.....

.....

.....

.....

.....

.....

5.

A car battery has an emf of 12.0 V. When the car is started the battery supplies a current of 120 A to the starter motor. The potential difference between the battery terminals [terminal pd] drops at this time to 8.4 V due to the internal resistance of the battery.

(a) Explain, in terms of energy,

(i) what is meant by 'an emf of 12.0 V', [2]

.....

.....

.....

(ii) why the terminal pd drops when the battery supplies a current. [1]

.....

.....

.....

(b) Calculate the internal resistance of the battery. [2]

.....

.....

.....

(c) The manufacturer warns against accidentally short-circuiting the battery. Calculate the current that would flow if the battery terminals were short-circuited with a spanner of negligible resistance. [1]

.....

.....

.....

(d) The battery will become 'flat' (i.e run out of energy) if it is continually run for a long period of time. It can then be fully recharged by a current of 3.0 A supplied for 16 hours.

(i) Calculate how much charge flows through the battery in this time. [2]

.....

.....

.....

(ii) Estimate how long the starter motor could be operated on a fully-charged battery. [1]

.....

6.

(a) Define the *emf* of a cell.

[2]


.....

.....

.....

(b) A student carries out an experiment to determine the *emf* and internal resistance of a cell. The pd across the cell is measured when it is supplying various currents. The following readings are obtained. Plot these results on the grid (pd on the *y*-axis and current on the *x*-axis) and draw a line through your points. [3]

| | | | | | |
|-------------|------|------|------|------|------|
| Current / A | 0.20 | 0.42 | 0.66 | 0.96 | 1.20 |
| pd / V | 1.31 | 1.13 | 0.93 | 0.68 | 0.48 |

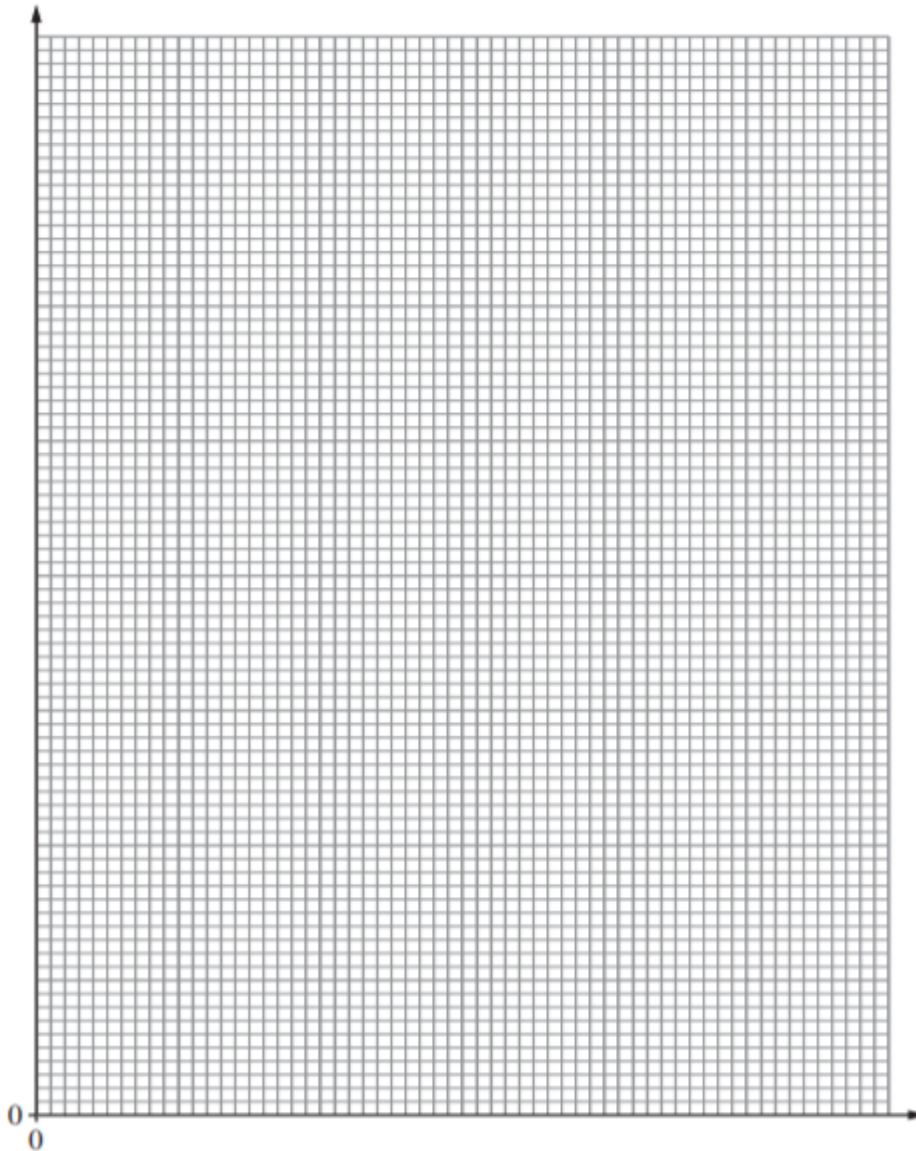

(c) Use your graph to determine:

(i) the emf of the cell; [1]

.....

(ii) the internal resistance of the cell. [2]

.....

.....

.....

(d) The cell is then connected to a torch bulb of resistance 6.0Ω for 20 minutes. Calculate the charge that flows through the bulb in this time. Assume the emf remains constant. [4]

.....

.....

.....

.....

.....


.....

.....

7.

(a) In the following circuits the resistance of X is **greater than** the resistance of Y.

Circuit A

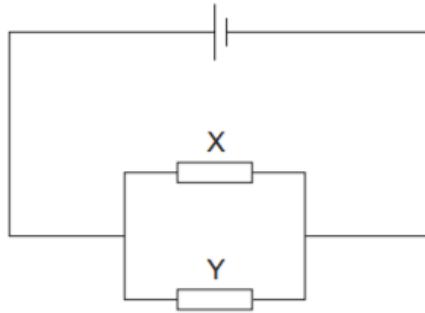

(i) For Circuit A, compare the current through, and the potential difference across X and Y. [1]

.....

.....

(ii)

Circuit B




For Circuit B, compare the current through, and the potential difference across X and Y. [1]

.....

.....

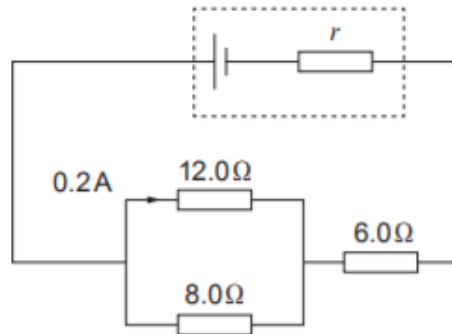- (b) The diagram below shows three resistors connected together as part of a circuit. The internal resistance, r , of the cell is also shown.



- (i) Show in clear steps that the current in the 8.0Ω resistor is 0.3A . [2]

.....

.....

.....

- (ii) Show that the potential difference across the combination of three resistors is 5.4V . [3]

.....

.....

.....

- (iii) Explain why the potential difference across the combination of three resistors is less than the emf of the cell. [2]

.....

.....

.....

- (iv) Calculate the internal resistance, r , of the cell given that its emf is 6.0V . [2]

.....

.....